

Lab 1:

The purpose of this lab is to learn how to use the field solver in ADS and use that to judge the accuracy of approximating calculators like PCB Toolkit from Saturn PCB and the online tool from Sierra Circuits.

Two step responses were tested. In both configurations, the source voltage was 2V, the source impedance was 50 Ohm, the load was an open, and the 10-90 rise time of the step was 50 psec. In the first configuration, a microstrip was tested with a height of 60 mils, a line width of 50 mils, a pour thickness of 1.4 mils (1 oz pour), and a substrate dielectric constant of 4.8. The second configuration was a symmetrical stripline with a height of 10 mils, a line width of 10 mils, a pour thickness of 0.7 mils (0.5 oz pour), and a dielectric constant of 4.6.

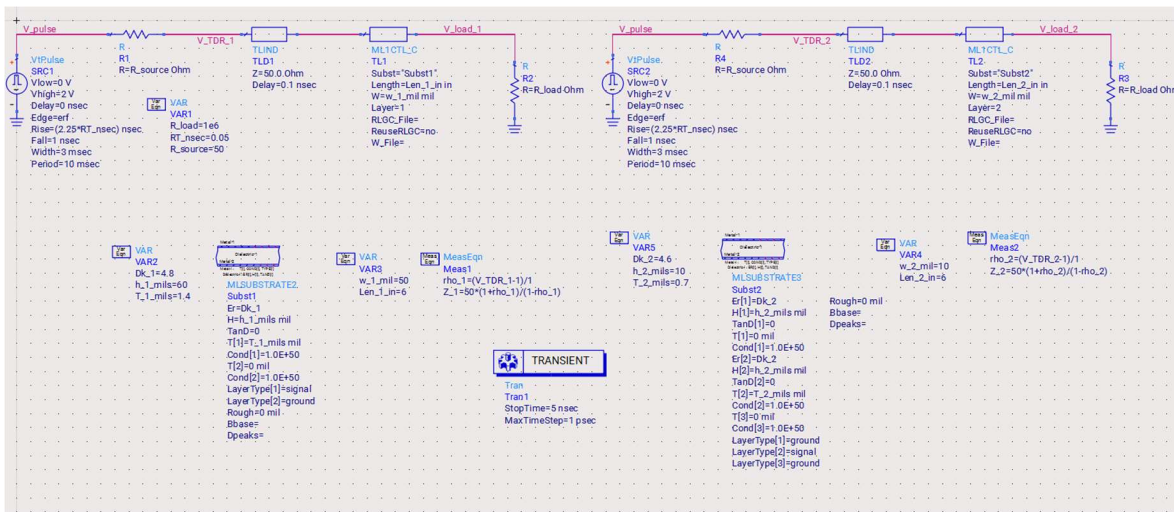


Figure 1: ADS schematic for testing the integrated 2D field solvers.

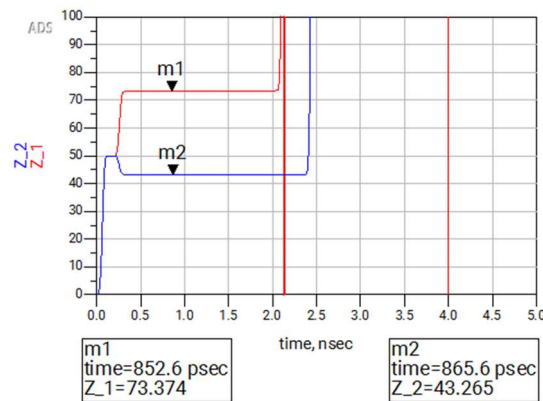


Figure 2: Simulated TDR for the transmission lines defined by the ADS 2D field solver. (Red=microstrip, blue=stripline).

These results show that the instantaneous impedance Z_0 is $\sim 73.4\Omega$ for the microstrip and $\sim 43.3\Omega$ for the stripline.

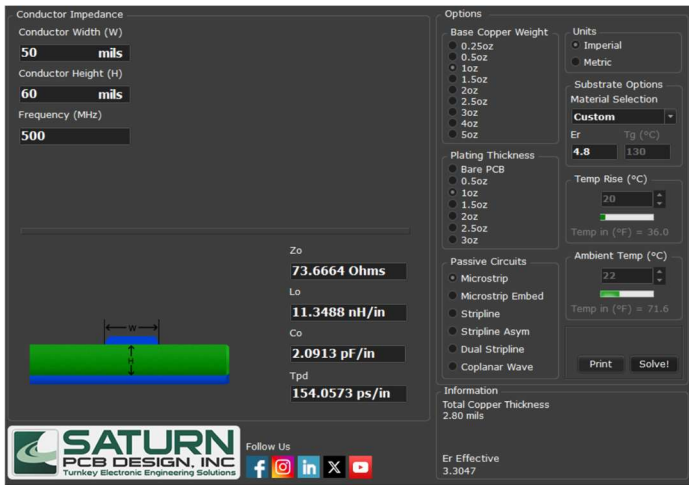


Figure 3: Saturn results for microstrip.

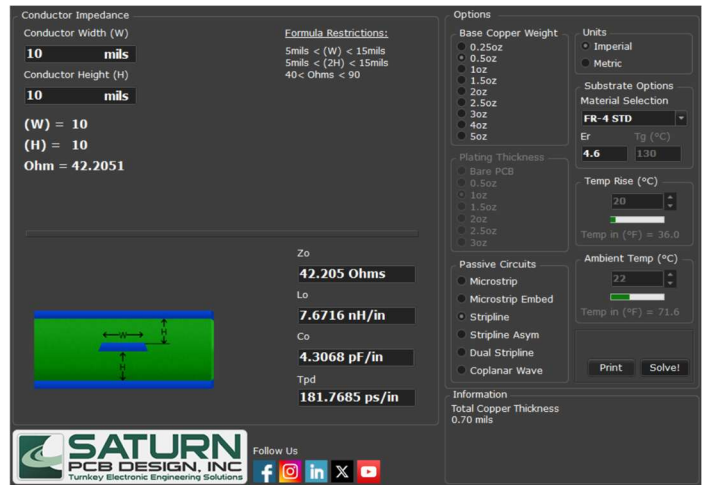


Figure 4: Saturn results for stripline.

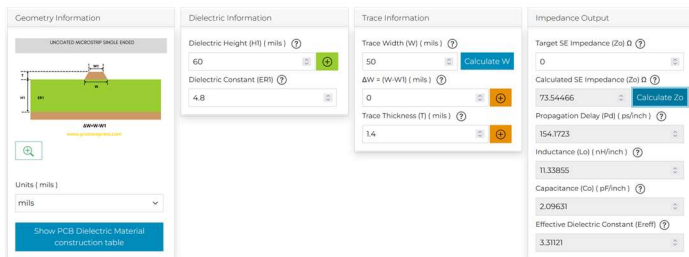


Figure 5: Sierra results for microstrip.

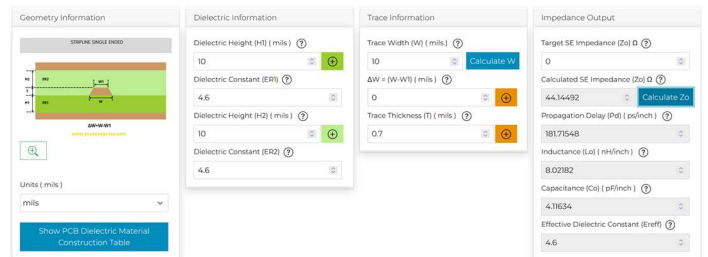


Figure 6: Sierra results for stripline.

Solver	Microstrip Z_0 (Ω)	Stripline Z_0 (Ω)
ADS	73.4	43.3
Saturn	73.7	42.2
Sierra	73.5	44.1

Table 1: Tabulated characteristic impedance results.

So what:

Based on the results in table 1, the estimator tools prove fairly accurate, but they do work better for the microstrip than for the stripline. I assume that this is because the equations get more complicated and harder to approximate when there are more layers.

Since using the ADS solver was so easy, I will not have much resistance to using it to get more accurate characteristic impedances. However, I do still need to build a circuit and simulate, so I will continue using the solvers when I need a quick answer or when the characteristic impedance isn't super important. If I don't have access to ADS, the results from the free estimators are close enough that I would feel comfortable using them for personal use cases.

Lab 2:

The purpose of this lab is to explore the impact of various termination strategies to mitigate reflections. The RX is open, the transmission line characteristics are common, and the voltage source is constant.

Three sources were tested (a clock, a step, and a single-bit response (SBR)) in conjunction with four termination strategies (no termination, source-series terminated, far-end ground terminated, and far-end V_{tt} terminated) for a total of 12 combinations.

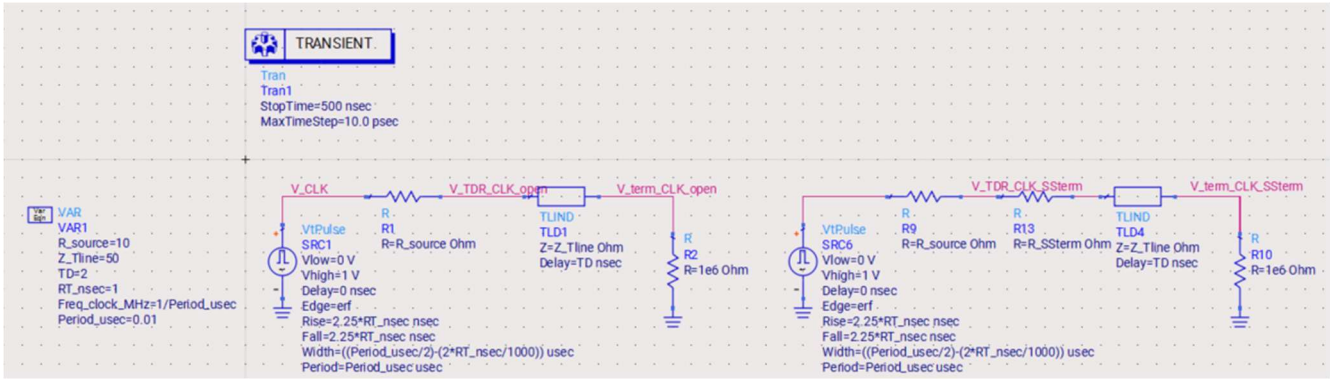


Figure 1: Portion of the ADS schematic for simulating the clock signal with no termination strategy and with source-series termination strategy. These termination strategies are copied onto other signal sources.

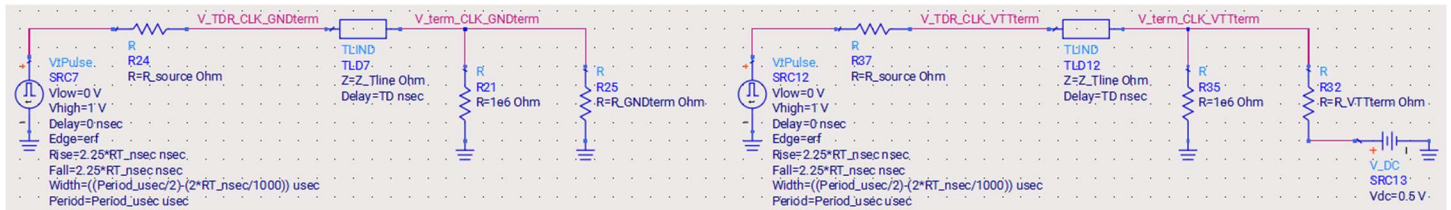


Figure 2: Portion of the ADS schematic for simulating the clock signal with far-end ground termination strategy and with far-end V_{tt} termination strategy. These termination strategies are copied onto other signal sources.

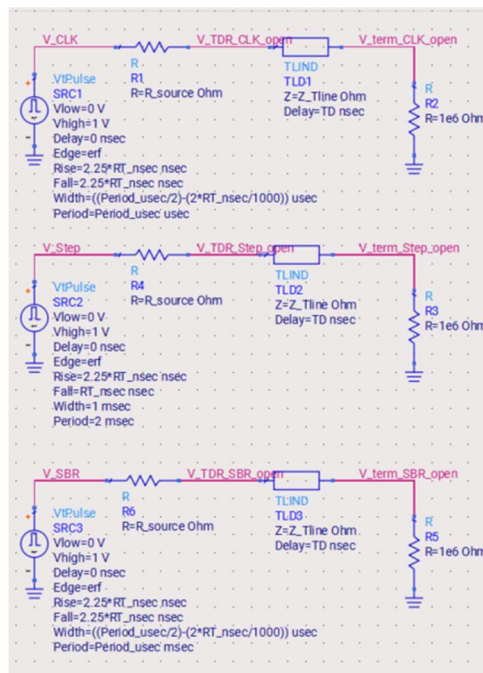


Figure 3: Portion of the ADS schematic showing the various sources without any termination strategy. The sources were copied for each termination strategy.

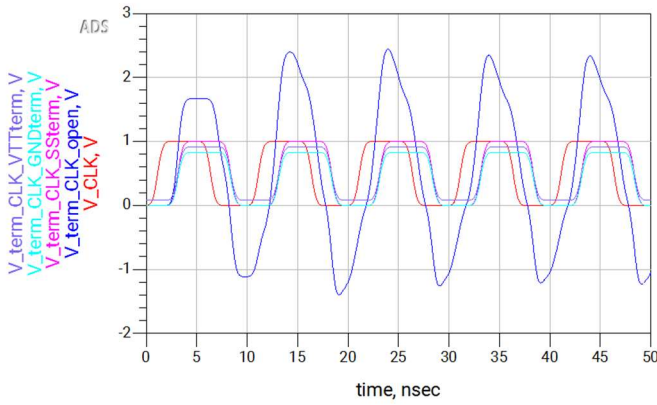


Figure 3: Termination results for the clock source.

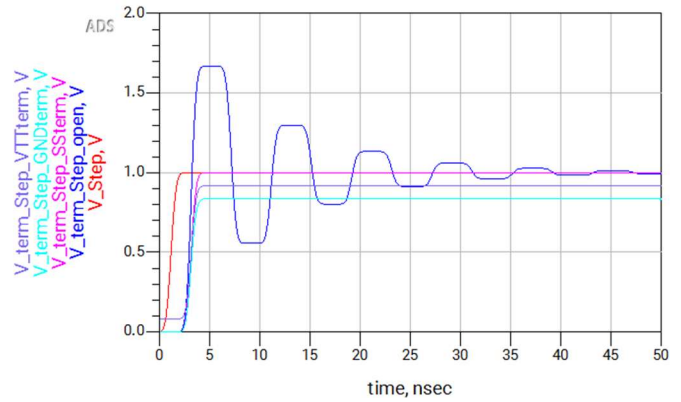


Figure 4: Termination results for the step source.

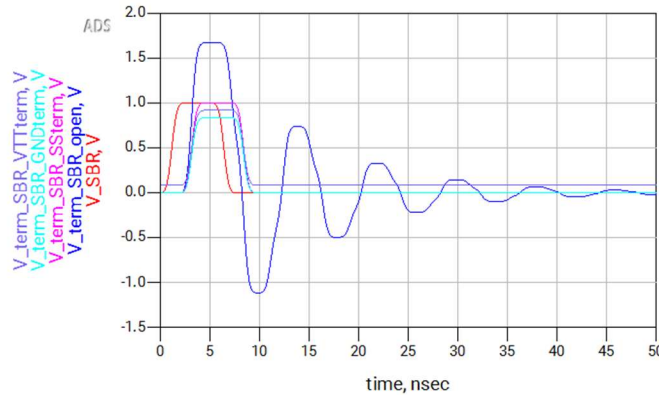


Figure 5: Termination results for the SBR source.

Based on the step, the response for an unterminated line takes ~30 nsec to settle, meaning it would create noise affecting the next two bits. This is an estimate and would vary depending on the margin of the RX.

All termination strategies show that they work to eliminate reflections at the RX end, though they all have different receiver voltage ranges. The source-series termination shows no voltage degradation due to the reflection at the RX. The far-end ground termination drops the high voltage by $V_{source} * \frac{Z_{tline} - R_{source}}{Z_{tline} + R_{source}} * 2 = 0.8V$. The far-end V_{tt} termination affects the low and high voltage. By setting $V_{tt} = 0.5 * V_{CC}$, the high voltage is 0.9V and the low voltage is 0.1V.

So what:

All of these termination strategies are valid. If having a reflection sent back through the transmission line to the source doesn't matter, I would prefer a source-series termination since it doesn't affect voltages at the receiving end. I like how the far-end V_{tt} termination can shift the voltages at the termination up or down so that the received voltage can be within the voltage range. I like the far-end ground termination because it is simple and doesn't require creating a V_{tt} source.